

# **CS 223 Digital Design**

Bilkent University

Fall 2024-25

## **Laboratory Assignment 3**

Digital Building Blocks: Decoders and MUXs in  
SystemVerilog

Nabeeha Khan

22301304


Section: 03

Date: 18<sup>th</sup> November 2024


# Multiplexer:

## 1) 3-to-1 Multiplexer:

### Graphical Symbol:

 

### Logic Diagram:

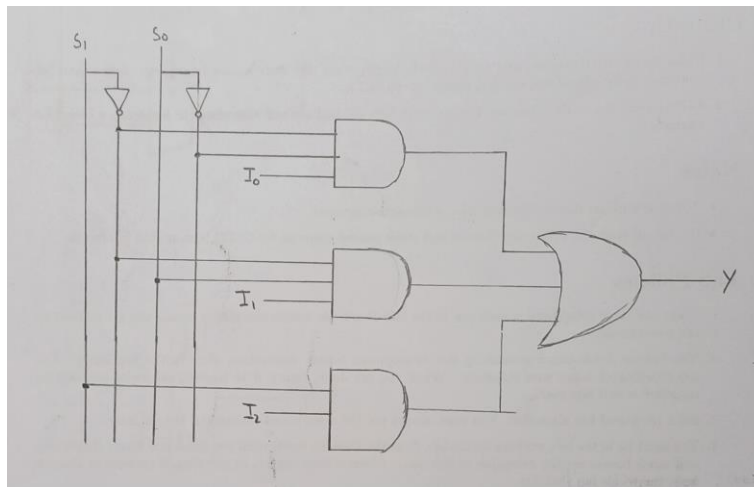

### Truth Table:

$S_1$	$S_0$	$Y$
0	0	$I_0$
0	1	$I_1$
1	X	$I_2$

### SystemVerilog Module:

```
module mux3to1(input logic I0, I1, I2, S0, S1, output logic Y);
```

```

    logic I0, I1, I2;

    assign I0 = ~S1 & ~S0 & I0;

    assign I1 = ~S1 & S0 & I1;

    assign I2 = S1 & I2;

    assign Y = I0 | I1 | I2;

endmodule

```

## **Testbench:**

```

module mux3to1_TB();

logic I0, I1, I2, S0, S1, Y;

mux3to1 dut(I0, I1, I2, S0, S1, Y);

initial begin

I0 = 0; I1 = 0; I2 = 0; S0 = 0; S1 = 0; #10;

I0 = 1; I1 = 0; I2 = 0; S0 = 0; S1 = 0; #10;

I0 = 0; I1 = 0; I2 = 0; S0 = 0; S1 = 1; #10;

I0 = 0; I1 = 1; I2 = 0; S0 = 0; S1 = 1; #10;

I0 = 0; I1 = 0; I2 = 0; S0 = 1; S1 = 0; #10;

I0 = 0; I1 = 0; I2 = 1; S0 = 1; S1 = 0; #10;

I0 = 0; I1 = 0; I2 = 0; S0 = 1; S1 = 1; #10;

I0 = 0; I1 = 0; I2 = 1; S0 = 1; S1 = 1; #10;


end

endmodule

```

## **2) 4-to-1 Multiplexer:**

### **Graphical Symbol:**

 

### Truth Table:

S <sub>1</sub>	S <sub>0</sub>	Y
0	0	I <sub>0</sub>
0	1	I <sub>1</sub>
1	0	I <sub>2</sub>
1	1	I <sub>3</sub>

### SystemVerilog Module:

```

module mux4to1(input logic I0, I1, I2, I3, S0, S1, output logic Y);
    logic l0, l1;
    assign l0 = (~S0 & I0) | (S0 & I1);
    assign l1 = (~S0 & I2) | (S0 & I3);
    assign Y = (~S1 & l0) | (S1 & l1);
endmodule

```

### Testbench:

```

module mux4to1_TB();
    logic I0, I1, I2, I3, S0, S1, Y;
    mux4to1 dut(I0, I1, I2, I3, S0, S1, Y);
    initial begin
        I0 = 0; I1 = 0; I2 = 0; I3 = 0; S0 = 0; S1 = 0; #10;
        I0 = 1; I1 = 0; I2 = 0; I3 = 0; S0 = 0; S1 = 0; #10;
    end
endmodule

```

```

I0 = 0; I1 = 0; I2 = 0; I3 = 0; S0 = 1; S1 = 0; #10;
I0 = 0; I1 = 1; I2 = 0; I3 = 0; S0 = 1; S1 = 0; #10;
I0 = 0; I1 = 0; I2 = 0; I3 = 0; S0 = 0; S1 = 1; #10;
I0 = 0; I1 = 0; I2 = 1; I3 = 0; S0 = 0; S1 = 1; #10;
I0 = 0; I1 = 0; I2 = 0; I3 = 0; S0 = 1; S1 = 1; #10;
I0 = 0; I1 = 0; I2 = 0; I3 = 1; S0 = 1; S1 = 1; #10;

end


endmodule

```

### 3) Implementation of f function:

 
#### Using 4-to-1 Mux:

We would require only one 4-to-1 mux and one inverter for this. We provide  $w_1$  and  $w_2$  as select inputs for the mux and pass  $w_3$  and its complement as the inputs to the mux so that we get  $\sim w_3$  for 00 and 11, and  $w_3$  for 01 and 10, and we get  $f$  as the output to this mux. The logic diagram will be as follows:


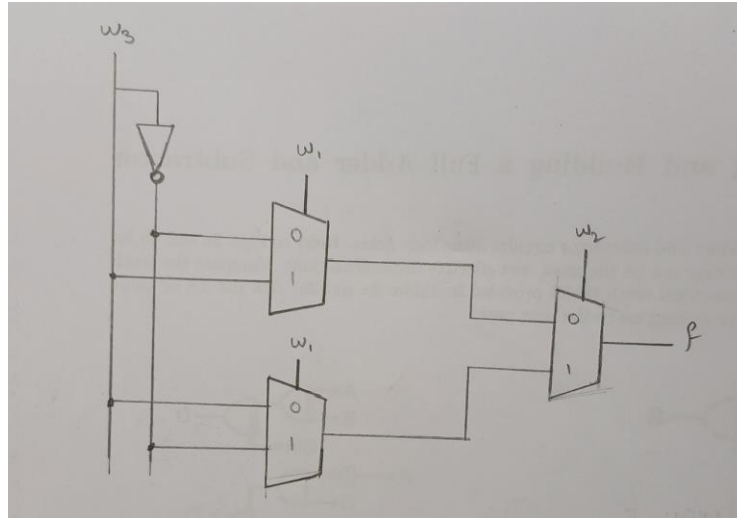
#### Using 2-to-1 Mux:

We would require three 2-to-1 mux and one inverter for this. We provide  $w_1$  as the select input for the first two mux. The first mux will get  $\sim w_3$  for 0 and  $w_3$  for 1 while the second mux will get  $w_3$  for 0 and  $\sim w_3$  for 1 as input. The result of both mux will go to a third mux, for which we provide  $w_2$  as select input, and it will pass the input of first mux for 0 and input of second mux for 1. The output of this final mux will yield function  $f$ . The logic diagram is as follows:




### Operation of function f:

Function f is based on the three input XNOR gate functionality i.e. it gives 1 when even number of inputs are 1 and 0 otherwise.

### 4) Implementation of g function:
 
#### Using 4-to-1 mux:

We would require a 4-to-1 mux and an inverter for this. We would provide  $w_1$  and  $w_2$  as the select input to the mux, and give  $w_3$  for 00 and 10 cases,  $\sim w_3$  for 01 case and  $V_{cc}$  (1) for 11 case. The output of the mux would yield function g. The logic diagram is as follows:




Modified truth table:

$w_1$	$w_2$	$g$
0	0	$w_3$

0	1	$\sim w_3$
1	0	$w_3$
1	1	1
 
## Using 2-to-1 mux and gates:

We can implement this function using a 2-to-1 mux, one XOR gate and one OR gate. Both XOR and OR gate will receive  $w_2$  and  $w_3$ . The mux will have  $w_1$  as control input and will pass output of XOR gate for 0 and output of OR for 1. The output of mux will give function  $g$ . The logic diagram is as follows:



Modified truth table:

$w_1$	$g$
0	$w_2 \wedge w_3$
1	$w_2 \mid w_3$

## SystemVerilog Module:

```
module gFunction(input logic w1, w2, w3, output logic g);
```

```
logic l0, l1, l2, l3;
```

```
assign l0 = w2 ^ w3;
```

```
assign l1 = w2 | w3;
```

```
assign l2 = l0 & ~w1;
```

```
assign l3 = l1 & w1;
```

```
assign g = l2 | l3;
```

```
endmodule
```

## Testbench:

```

module gFunction_TB();
logic w1, w2, w3, g;
gFunction mod(w1, w2, w3, g);
initial begin
w1 = 0; w2 = 0; w3 = 0; #10;
        w1 = 0; w2 = 0; w3 = 1; #10;


w1 = 0; w2 = 1; w3 = 0; #10;
w1 = 0; w2 = 1; w3 = 1; #10;
w1 = 1; w2 = 0; w3 = 0; #10;
w1 = 1; w2 = 0; w3 = 1; #10;
w1 = 1; w2 = 1; w3 = 0; #10;
w1 = 1; w2 = 1; w3 = 1; #10;
end
endmodule

```

## Decoder:


### 1. 2-to-4 Decoder:

#### Graphical Symbol:

 

#### Logic Diagram:



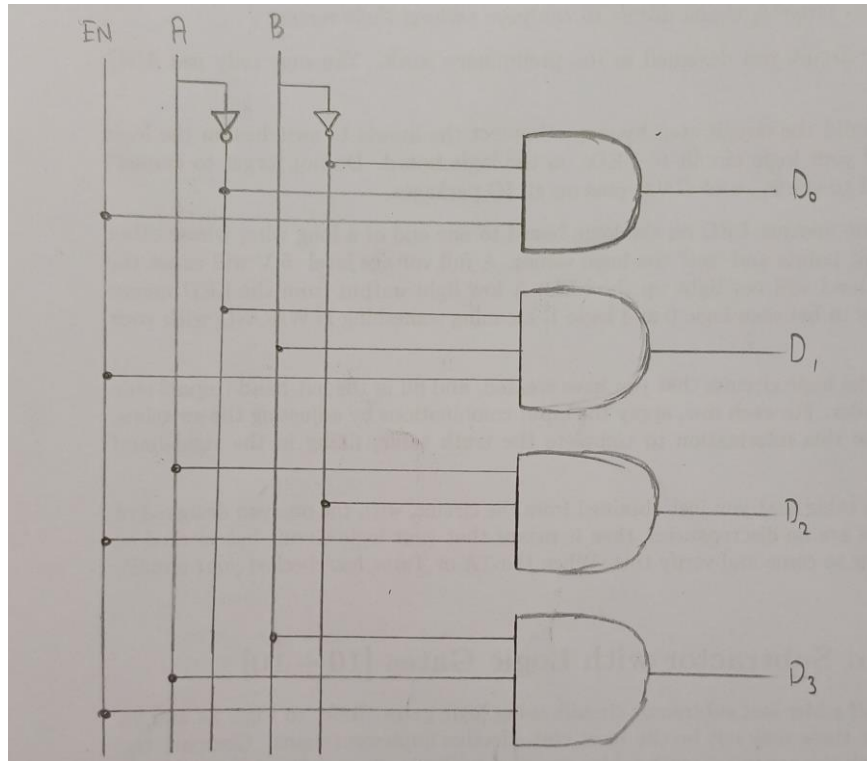

### Truth Table:

A	B	EN	D <sub>0</sub>	D <sub>1</sub>	D <sub>2</sub>	D <sub>3</sub>
X	X	0	0	0	0	0
0	0	1	1	0	0	0
0	1	1	0	1	0	0
1	0	1	0	0	1	0
1	1	1	0	0	0	1

### SystemVerilog Module:

```

module decoder2to4(input logic A, B, EN, output logic D0, D1, D2, D3);
    assign D0 = ~A & ~B & EN;
    assign D1 = ~A & B & EN;
    assign D2 = A & ~B & EN;
    assign D3 = A & B & EN;
endmodule

```

### Testbench:


```

module decoder2to4_TB();
logic A, B, EN, D0, D1, D2, D3;
decoder2to4 mod(A, B, EN, D0, D1, D2, D3);
initial begin
A = 0; B = 0; EN = 0; #10;
A = 0; B = 1; EN = 0; #10;
A = 1; B = 0; EN = 0; #10;
A = 1; B = 1; EN = 0; #10;
A = 0; B = 0; EN = 1; #10;
A = 0; B = 1; EN = 1; #10;
A = 1; B = 0; EN = 1; #10;
A = 1; B = 1; EN = 1; #10;
end
endmodule

```

## 2. 3-to-8 Decoder:

### Logic Diagram:

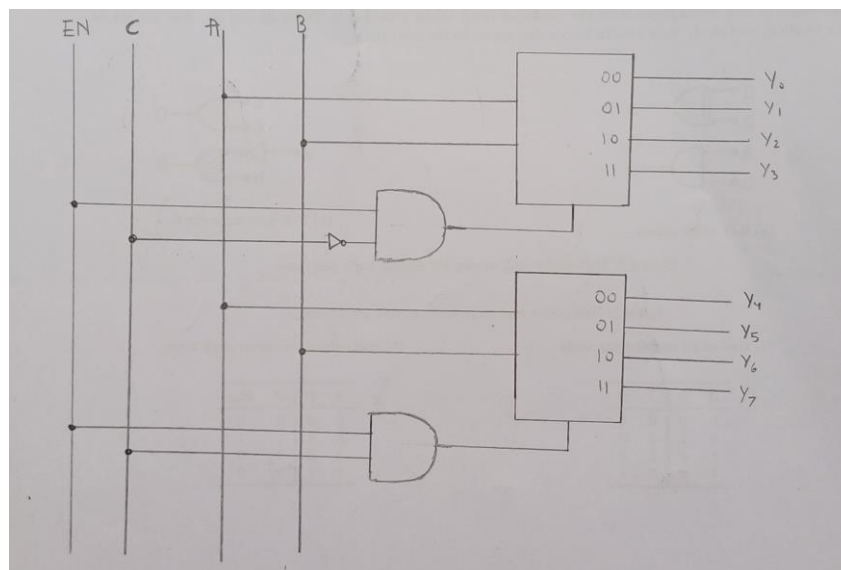

### SystemVerilog Module:

```

module decoder3to8(input logic A, B, C, EN, output logic Y0, Y1, Y2, Y3, Y4, Y5, Y6, Y7);
logic en1, en2;

    assign en1 = EN & ~C;

    decoder2to4 decoder1(A, B, en1, Y0, Y1, Y2, Y3);

    assign en2 = EN & C;

    decoder2to4 decoder2(A, B, en2, Y4, Y5, Y6, Y7);

endmodule

```

## Testbench:

```

module decoder3to8_TB();

logic A, B, C, EN, Y0, Y1, Y2, Y3, Y4, Y5, Y6, Y7;

    decoder3to8 mod(A, B, C, EN, Y0, Y1, Y2, Y3, Y4, Y5, Y6, Y7);

    initial begin

        A = 0 ; B = 0 ; C = 0 ; EN = 0 ; #10 ;
        A = 1 ; B = 0 ; C = 0 ; EN = 0 ; #10 ;
        A = 0 ; B = 1 ; C = 0 ; EN = 0 ; #10 ;
        A = 1 ; B = 1 ; C = 0 ; EN = 0 ; #10 ;
        A = 0 ; B = 0 ; C = 1 ; EN = 0 ; #10 ;
        A = 1 ; B = 0 ; C = 1 ; EN = 0 ; #10 ;
        A = 0 ; B = 1 ; C = 1 ; EN = 0 ; #10 ;
        A = 1 ; B = 1 ; C = 1 ; EN = 0 ; #10 ;
        A = 0 ; B = 0 ; C = 0 ; EN = 1 ; #10 ;
        A = 1 ; B = 0 ; C = 0 ; EN = 1 ; #10 ;
        A = 0 ; B = 1 ; C = 0 ; EN = 1 ; #10 ;
        A = 1 ; B = 1 ; C = 0 ; EN = 1 ; #10 ;
        A = 0 ; B = 0 ; C = 1 ; EN = 1 ; #10 ;
        A = 1 ; B = 0 ; C = 1 ; EN = 1 ; #10 ;
        A = 0 ; B = 1 ; C = 1 ; EN = 1 ; #10 ;

    end

```

```

        A = 1 ; B = 1 ; C = 1 ; EN = 1 ; #10 ;

    end


endmodule

```

## Logic Function:

### 1. 8-to-1 Mux:

#### Schematic Diagram:

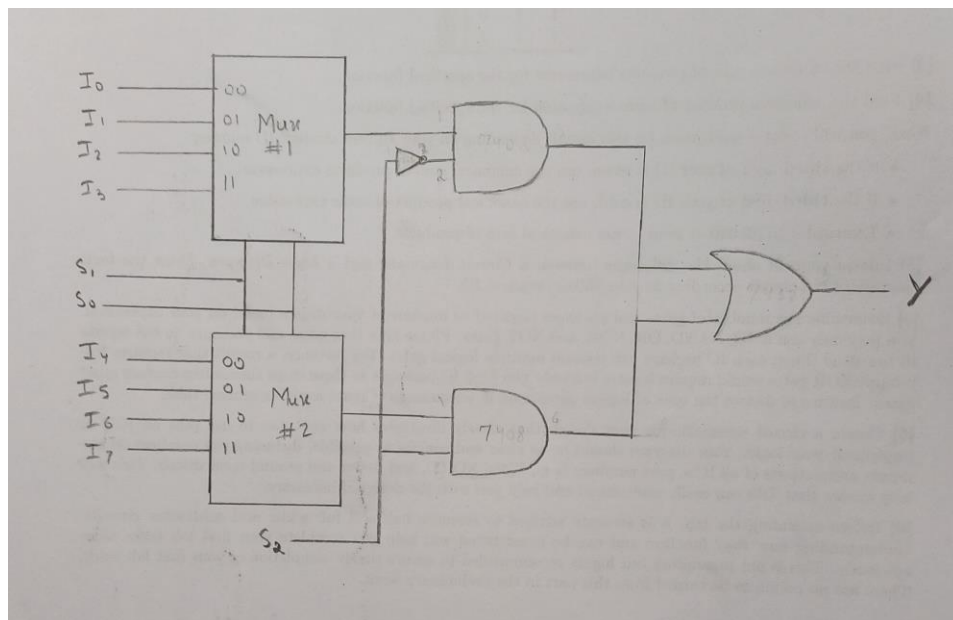

#### SystemVerilog Module:

```

module mux8to1(input logic I0, I1, I2, I3, I4, I5, I6, I7, S2, S1, S0, output logic Y);
    logic l1, l2, l3, l4;

    mux4to1 mux1(I0, I1, I2, I3, S1, S0, l1);
    mux4to1 mux2(I4, I5, I6, I7, S1, S0, l2);

    assign l3 = l1 & ~S2;
    assign l4 = l2 & S2;

    assign Y = l3 | l4;

endmodule


```

## Testbench:

```
module mux8to1_TB();  
logic I0, I1, I2, I3, I4, I5, I6, I7, S2, S1, S0, Y;  
mux8to1 mod(I0, I1, I2, I3, I4, I5, I6, I7, S2, S1, S0, Y);  
initial begin  
    I0 = 0; I1 = 0; I2 = 0; I3 = 0; I4 = 0; I5 = 0; I6 = 0; I7 = 0; S2 = 0; S1 = 0; S0 = 0; #10;  
    I0 = 1; I1 = 0; I2 = 0; I3 = 0; I4 = 0; I5 = 0; I6 = 0; I7 = 0; S2 = 0; S1 = 0; S0 = 0; #10;  
    I0 = 0; I1 = 0; I2 = 0; I3 = 0; I4 = 0; I5 = 0; I6 = 0; I7 = 0; S2 = 0; S1 = 0; S0 = 1; #10;  
    I0 = 0; I1 = 1; I2 = 0; I3 = 0; I4 = 0; I5 = 0; I6 = 0; I7 = 0; S2 = 0; S1 = 0; S0 = 1; #10;  
    I0 = 0; I1 = 0; I2 = 0; I3 = 0; I4 = 0; I5 = 0; I6 = 0; I7 = 0; S2 = 0; S1 = 1; S0 = 0; #10;  
    I0 = 0; I1 = 0; I2 = 1; I3 = 0; I4 = 0; I5 = 0; I6 = 0; I7 = 0; S2 = 0; S1 = 1; S0 = 0; #10;  
    I0 = 0; I1 = 0; I2 = 0; I3 = 0; I4 = 0; I5 = 0; I6 = 0; I7 = 0; S2 = 0; S1 = 1; S0 = 1; #10;  
    I0 = 0; I1 = 0; I2 = 0; I3 = 1; I4 = 0; I5 = 0; I6 = 0; I7 = 0; S2 = 0; S1 = 1; S0 = 1; #10;  
    I0 = 0; I1 = 0; I2 = 0; I3 = 0; I4 = 0; I5 = 0; I6 = 0; I7 = 0; S2 = 1; S1 = 0; S0 = 0; #10;  
    I0 = 0; I1 = 0; I2 = 0; I3 = 0; I4 = 1; I5 = 0; I6 = 0; I7 = 0; S2 = 1; S1 = 0; S0 = 0; #10;  
    I0 = 0; I1 = 0; I2 = 0; I3 = 0; I4 = 0; I5 = 0; I6 = 0; I7 = 0; S2 = 1; S1 = 0; S0 = 1; #10;  
    I0 = 0; I1 = 0; I2 = 0; I3 = 0; I4 = 0; I5 = 1; I6 = 0; I7 = 0; S2 = 1; S1 = 0; S0 = 1; #10;  
    I0 = 0; I1 = 0; I2 = 0; I3 = 0; I4 = 0; I5 = 0; I6 = 0; I7 = 0; S2 = 1; S1 = 1; S0 = 0; #10;  
    I0 = 0; I1 = 0; I2 = 0; I3 = 0; I4 = 0; I5 = 0; I6 = 1; I7 = 0; S2 = 1; S1 = 1; S0 = 0; #10;  
    I0 = 0; I1 = 0; I2 = 0; I3 = 0; I4 = 0; I5 = 0; I6 = 0; I7 = 0; S2 = 1; S1 = 1; S0 = 1; #10;  
    I0 = 0; I1 = 0; I2 = 0; I3 = 0; I4 = 0; I5 = 0; I6 = 0; I7 = 1; S2 = 1; S1 = 1; S0 = 1; #10;  
end  
endmodule
```

## 2. Five Input Function:

### Schematic Diagram:

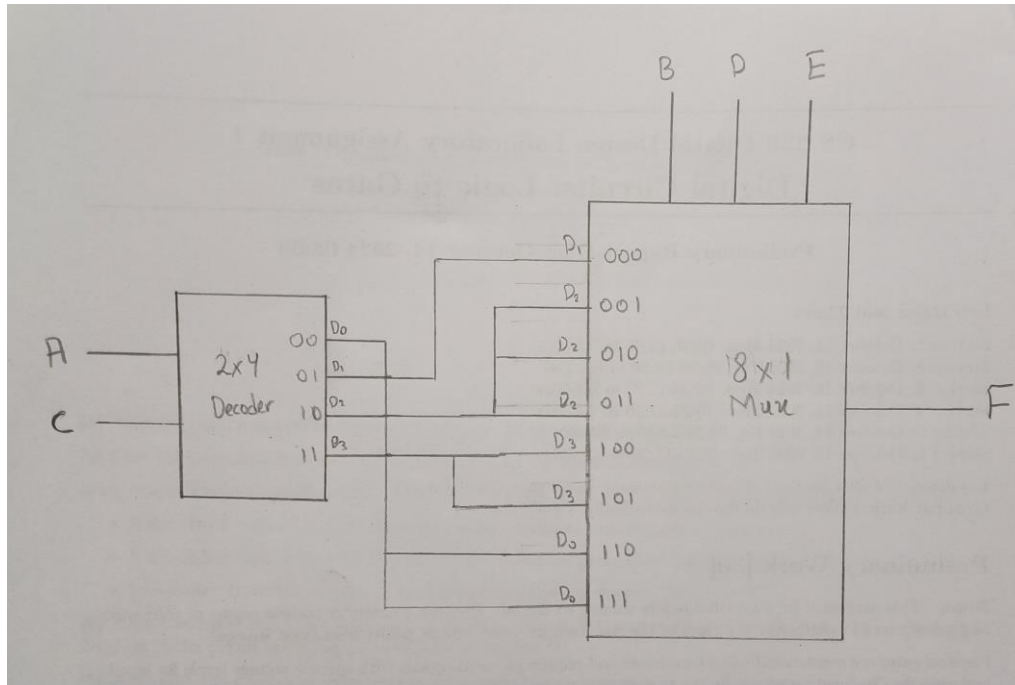

## SystemVerilog Module:

```

module Ffunction(input logic A, B, C, D, E, output logic F);
    logic EN, D0, D1, D2, D3;
    assign EN = 1'b1;
    decoder2to4 decoder(A, C, EN, D0, D1, D2, D3);
    mux8to1 mux(D1, D2, D2, D2, D3, D3, D0, D0, B, D, E, F);
endmodule

```