

CS 223 Digital Design

Bilkent University

Fall 2024-25

Laboratory Assignment 5

Traffic Light System and Gray Code Counter

Nabeeha Khan


22301304

Section: 03

Date: 9th December 2024

Traffic Light System:

1. State Transition Diagram:

 

2. State Encodings:

Current State S	Encodings S _{2:0}
S ₀	000
S ₁	001
S ₂	010
S ₃	011
S ₄	100
S ₅	101
S ₆	110
S ₇	111

3. State Transition Table:

Current State			Inputs		Next State		
S ₂	S ₁	S ₀	S _A	S _B	S' ₂	S' ₁	S' ₀
0	0	0	X	0	0	0	0
0	0	0	X	1	0	0	1
0	0	1	X	X	0	1	0
0	1	0	X	X	0	1	1
0	1	1	X	X	1	0	0
1	0	0	0	X	1	0	0
1	0	0	1	X	1	0	1
1	0	1	X	X	1	1	0

1	1	0	X	X	1	1	1
1	1	1	X	X	0	0	0

4. Output Encodings:

Output	Encodings $L_{2:0}$
Red	111
Yellow	001
Green	011

5. Output Table:

Current State			Output					
S_2	S_1	S_0	L_{A2}	L_{A1}	L_{A0}	L_{B2}	L_{B1}	L_{B0}
0	0	0	0	1	1	1	1	1
0	0	1	0	0	1	1	1	1
0	1	0	1	1	1	1	1	1
0	1	1	1	1	1	0	0	1
1	0	0	1	1	1	0	1	1
1	0	1	1	1	1	0	0	1
1	1	0	1	1	1	1	1	1
1	1	1	0	0	1	1	1	1

6. Next State and Output Equations:

Next State:

$$S'_2 = S_2 S_0' + S_2' S_1 S_0 + S_2 S_1'$$

$$S'_1 = S_1 \oplus S_0$$

$$S'_0 = S_1 S_0' + S_2' S_1' S_0' S_B + S_2 S_1' S_0' S_A$$

Output:

$$L_{A2} = S_2 \oplus S_1 + S_2 S_0'$$

$$L_{A1} = S_0' + S_2 \oplus S_1$$

$$L_{A0} = 1$$


$$L_{B2} = S_1 S_0' + (S_2 \oplus S_1)'$$

$$L_{B1} = S_0' + (S_2 \oplus S_1)'$$


$L_{B0} = 1$

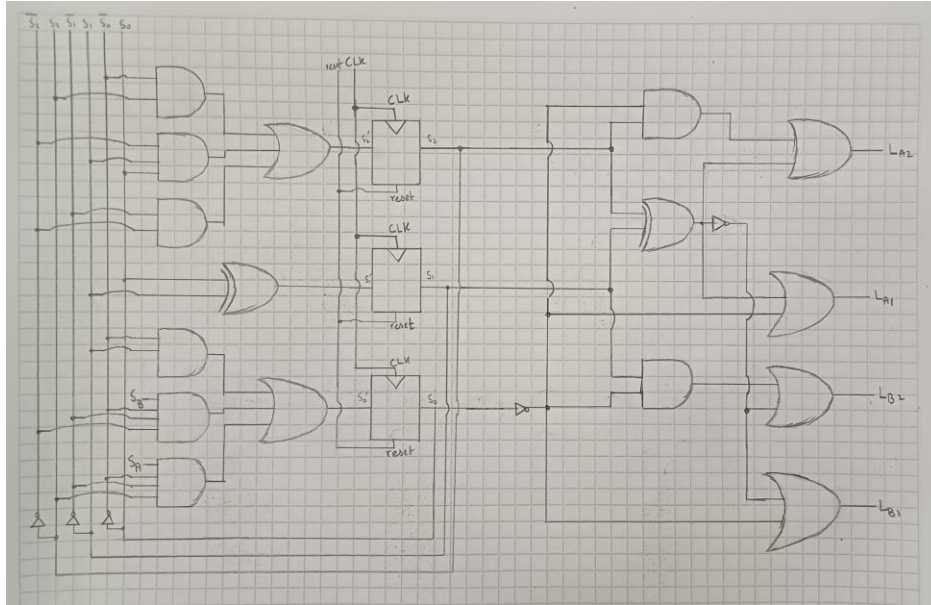7. FSM Schematic:

We would need **3 Flip-flops** for this schematic.



8. FSM Schematic using Decoders:

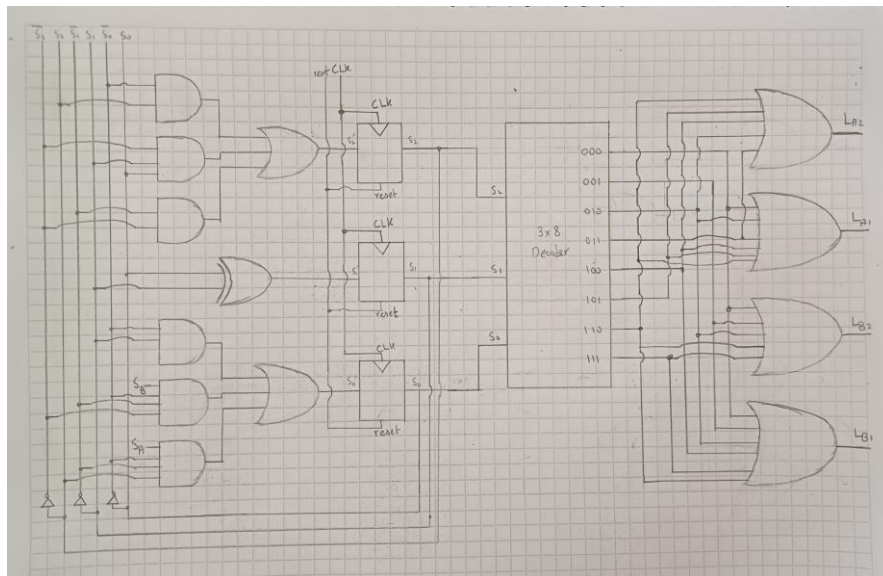

9. SystemVerilog Module and Testbench:

```
//Module for clock divider
```

```
module clock_cycle( input logic clk, output logic clk_div );
```

```
localparam constantNumber = 150000000;  
logic [31:0] count;
```

```
always @(posedge(clk))  
begin  
if (count == constantNumber - 1)  
    count <= 32'b0;  
    else  
        count <= count + 1;  
end
```

```
always @ (posedge(clk))  
begin  
    if (count == constantNumber - 1)  
        clk_div <= ~clk_div;  
    else  
        clk_div <= clk_div;  
end
```

```
endmodule
```

```
//Module for Traffic Lights System
```

```
module TrafficLights(input logic clk, reset, sa, sb,  
                    output logic [2:0] la, lb);
```

```
    logic clkslow;
```

```
    clock_cycle clksl(clk, clkslow);
```

```
    typedef enum logic [2:0] {s0, s1, s2, s3, s4, s5, s6, s7} Statetype;
```

```
    Statetype [1:0] state, nextstate;
```

```
    parameter g = 3'b011;
```

```
    parameter y = 3'b001;
```

```
    parameter r = 3'b111;
```

```
    always_ff @(posedge clkslow, posedge reset)
```

```
        if(reset) state <= s0;
```

```
    else state <= nextstate;
```

```
always_comb
```

```
case(state)
```

```
    s0: if(sb) nextstate = s1;
```

```
        else nextstate = s0;
```

```
    s1:    nextstate = s2;
```

```
    s2:    nextstate = s3;
```

```
    s3:    nextstate = s4;
```

```
    s4: if(sa) nextstate = s5;
```

```
        else nextstate = s4;
```

```
    s5:    nextstate = s6;
```

```
    s6:    nextstate = s7;
```

```
    s7:    nextstate = s0;
```

```
    default: nextstate = s0;
```

```
endcase
```

```
always_comb
```

```
case(state)
```

```
    s0:    {la, lb} = {g, r};
```

```
    s1:    {la, lb} = {y, r};
```

```
    s2:    {la, lb} = {r, r};
```

```
    s3:    {la, lb} = {r, y};
```

```
    s4:    {la, lb} = {r, g};
```

```
    s5:    {la, lb} = {r, y};
```

```
    s6:    {la, lb} = {r, r};
```

```
    s7:    {la, lb} = {y, r};
```

```
    default: {la, lb} = {g, r};
```

```
endcase
```

```
endmodule
```

```

//Testbench
module TrafficLight_TB();
    logic clk, reset, sa, sb;
    logic [2:0] la;
    logic [2:0] lb;

    TrafficLights dut(clk, reset, sa, sb, la, lb);

    always
    begin
        clk <= 1; #5;
        clk <= 0; #5;
    end

    initial
    begin
        reset <= 1; #20;
        reset <= 0; #20;
        sa <= 1; sb <= 0; #100;
        sa <= 0; sb <= 0; #100;
        sa <= 0; sb <= 1; #100;
        sa <= 1; sb <= 1; #100;
    end
endmodule

```

Grey Code:

1. Algorithm for n-bit Grey Code:

To generate a n-bit grey code recursively, we have two steps: base case and recursive step. For base case which is set at $n = 1$, we return an array of strings "0" and "1". In recursive step, which is for $n > 1$, we call the function again for $n - 1$ which produces an array of n-1 bit grey code as strings, then we append this array first with "0" in the same order they appear in array to get array1 and then append with "1" in reverse order they appear in array to get array2. Then we return array1 + array2, which is the array of n bit grey code. The pseudo code is given below:

```
GreyCode(n)

if n = 1: return ["0", "1"]

else: prevGrey = GreyCode(n - 1)

        array1 = ["0" + prevGrey[n-2: 0] ]
        array2 = ["1" + prevGrey[0: n-2] ]

return array1+array2
```

2. SystemVerilog Module for 4-bit Grey Code:

```
//Module for clock divider

module clock_cycle1Hz (input logic clk, output logic clk_div );

localparam constantNumber = 50000000;
logic [31:0] count;

always @(posedge clk)
begin
    if (count == constantNumber - 1)
        count <= 32'b0;
    else
        count <= count + 1;
end

always @(posedge clk)
begin
    if (count == constantNumber - 1)
        clk_div <= ~clk_div;
    else
        clk_div <= clk_div;
end

endmodule

//Module for upcounter register
```



```
module upcountRegister(  
    input logic clk, reset, load_en, enable,  
    input logic [3:0] load,  
    output logic [3:0] q  
);
```

```
    always_ff @(posedge clk) begin  
        if(reset)  
            q <= 4'b0;  
        else if(load_en)  
            q <= load;  
        else if(enable)  
            q <= q + 1;  
    end  
endmodule
```

//Module for binary to grey code converter

```
module binaryToGrey(  
    input logic [3:0] binary,  
    output logic [3:0] grey  
);  
  
    always_comb begin  
        grey[3] = binary[3];  
        grey[2] = binary[3] ^ binary[2];  
        grey[1] = binary[2] ^ binary[1];  
        grey[0] = binary[1] ^ binary[0];  
    end  
endmodule
```

```

//Module for 4-bit Grey code up counter

module greyCode4bit( input logic clk, reset, load_en, enable, input logic [3:0] load, output logic
[3:0] grey );

logic clk_slow;
clock_cycle1Hz clockdiv(clk, clk_slow);

logic [3:0] binary;
upcountRegister register(clk_slow, reset, load_en, enable, load, binary);

binaryToGrey converter(binary, grey);

endmodule


//Testbench

module grayCode4bit_TB();

logic clk, reset, load_en, enable;
logic [3:0] load;
logic [3:0] grey;

grayCode4bit uut (clk, reset, load_en, enable, load, grey);

initial clk = 0;
always #5 clk = ~clk;

initial begin
    reset = 1; enable = 0; load_enable = 0; load = 4'b0; #10;
    reset = 0; #10;
    enable = 1; #100;

    load = 4'b0010; load_enable = 1; #10;
    load = 4'b1111; load_enable = 1; #10;
    load = 4'b0111; load_enable = 1; #10;
    load_enable = 0; #50
end

endmodule

```

3. SystemVerilog Module for 8-bit Grey Code:

```

//Module for clock divider

module clock_cycle1Hz (input logic clk, output logic clk_div );

```

```
localparam constantNumber = 500000000;  
logic [31:0] count;
```

```
always @(posedge clk)  
begin  
    if (count == constantNumber - 1)  
        count <= 32'b0;  
    else  
        count <= count + 1;  
end
```

```
always @(posedge clk)  
begin  
    if (count == constantNumber - 1)  
        clk_div <= ~clk_div;  
    else  
        clk_div <= clk_div;  
end
```

```
endmodule
```

```
//Module for upcounter register
```

```
module upcountRegister(  
    input logic clk, reset, load_en, enable,  
    input logic [7:0] load,  
    output logic [7:0] q  
);
```

```
always_ff @(posedge clk) begin  
    if(reset)  
        q <= 8'b0;  
    else if(load_en)  
        q <= load;  
    else if(enable)  
        q <= q + 1;  
end
```

```
endmodule
```

```
//Module for binary to grey code converter
```

```
module binaryToGrey(
```

```
    input logic [7:0] binary,
```

```
    output logic [7:0] grey
```

```
);
```

```
    always_comb begin
```

```
        grey[7] = binary[7];
```

```
        grey[6] = binary[7] ^ binary[6];
```

```
        grey[5] = binary[6] ^ binary[5];
```

```
        grey[4] = binary[5] ^ binary[4];
```

```
        grey[3] = binary[4] ^ binary[3];
```

```
        grey[2] = binary[3] ^ binary[2];
```

```
        grey[1] = binary[2] ^ binary[1];
```

```
        grey[0] = binary[1] ^ binary[0];
```

```
    end
```

```
endmodule
```

```
//Module for 8-bit Grey code up counter
```

```
module greyCode8bit( input logic clk, reset, load_en, enable,
```

```
    input logic [7:0] load,
```

```
    output logic [7:0] grey
```

```
);
```

```
    logic clk_slow;
```

```
    clock_cycle1Hz clockdiv(clk, clk_slow);
```

```
    logic [7:0] binary;
```

```
    upcountRegister register(clk_slow, reset, load_en, enable, load, binary);
```

```
    binaryToGrey converter(binary, grey);
```

```
endmodule
```

```

//Testbench

module grayCode8bit_TB();

logic clk, reset, load_en, enable;
logic [7:0] load;
logic [7:0] grey;

grayCode8bit uut (clk, reset, load_en, enable, load, grey);

initial clk = 0;
always #5 clk = ~clk;

initial begin
    reset = 1; enable = 0; load_en = 0; load = 8'b0; #10;
    reset = 0; #10;
    enable = 1; #100;

    load = 4'b00011010; load_en = 1; #10
    load = 4'b00001111; load_en = 1; #10;
    load = 4'b10000000; load_en = 1; #10;
    load_en = 0; #50
end

endmodule

```